

# CS2022 Computer Architecture

Michael Manzke

## Project 1 -Datapath Design -Part A

8 February 2018

### Description:

The circuit overleaf implements a 4-bit version of the Register file section of the datapath shown in Mano and Kime figure 7-9 (or 4th lecture, page 12), by using components designed in VHDL and connected at the top-level through a schematic.

1. Design the VHDL components (Register, Decoder, and two Multiplexer 16 bit) and interconnect them to build a register file. The schematic shows only four registers. Your solution should implement eight registers.
2. You should provide test benches and simulations that prove the correctness of the following operations:
  - a. Correctly load an arbitrary HEX value into each of the eight registers, i.e. that it can execute the transfers  $R_i \leftarrow X_i$   $i=0,7$
  - b. Correctly transfer the contents of any register to any other register, i.e. that it can execute the transfers  $R_i \leftarrow R_j$ ,  $i,j=0,7$

**DUE: Friday, 16<sup>th</sup> February 2018**

Please submit a copy of your VHDL-code and test-benches including all simulation results to Blackboard.

