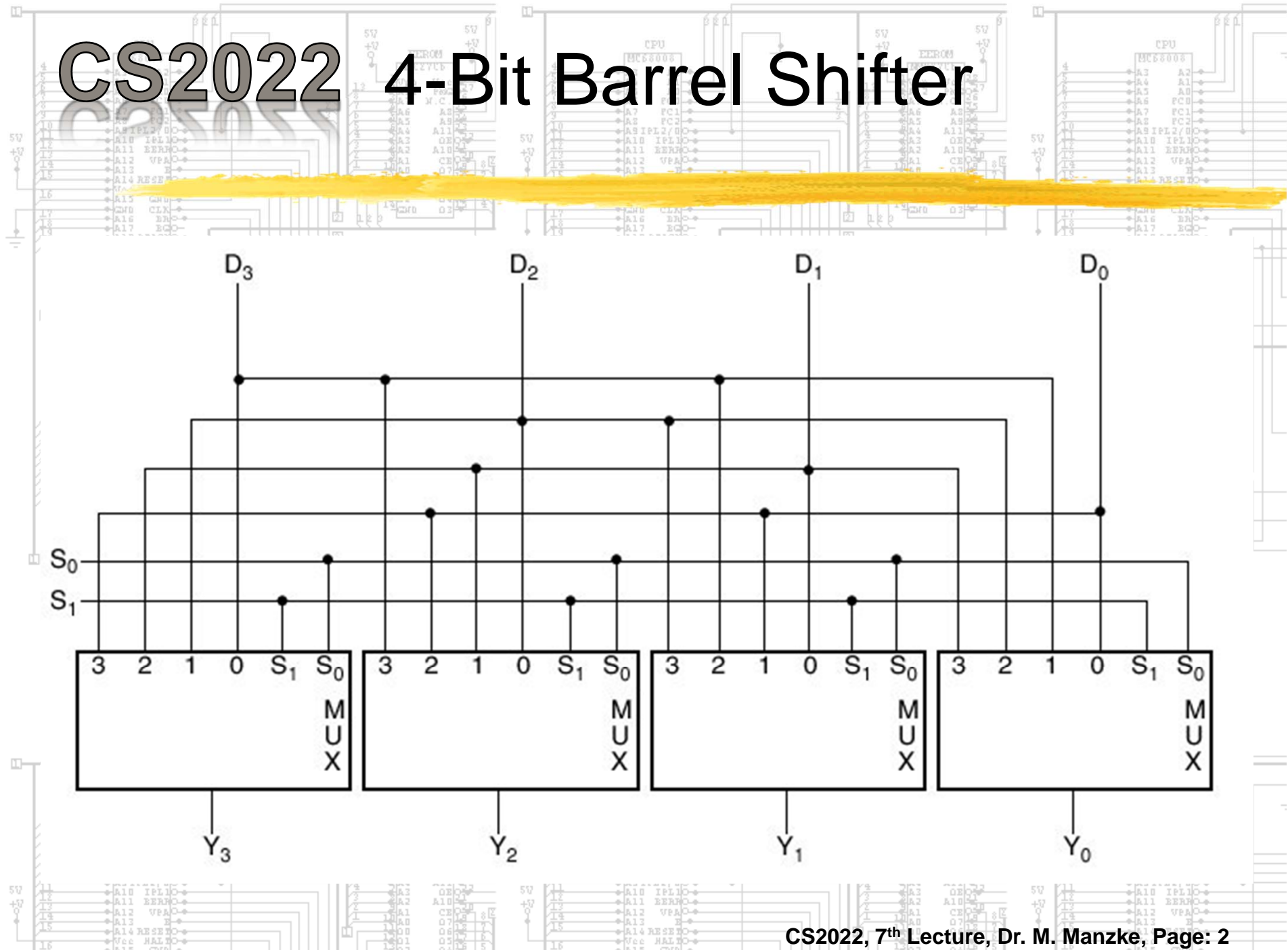


CS2022 Shift Operations

By controlling IR and IL with multiplexers it is straightforward to adapt this circuit to perform arithmetic shifts, constructive and destructive shifts, Rotates and rotate-then-carry operation

CS2022 4-Bit Barrel Shifter



CS2022 Multiple Shifts

► If multiple shifts are required we wire them into multiplexers that have an input for every bit on the bus to obtain a Barrel shifter (Previous slide).

S_1	S_2	Y_3	Y_2	Y_1	Y_0	Micro-ops
0	0	D_3	D_2	D_1	D_0	No Rotate
0	1	D_2	D_1	D_0	D_3	Rotate One
1	0	D_1	D_0	D_3	D_2	Rotate Two
1	1	D_0	D_3	D_2	D_1	Rotate Three

CS2022 Controlling a Datapath


The Control Word

- ▶ The figure on the next slide is an updated version of our introductory datapath (4th Lecture, Page 12) where the register file has been expanded to a more realistic eight n-bit registers.
- ▶ Consequently the destination decoder and A and B bus MUX require three-bit select input.
- ▶ The Function Unit still requires five bits to select ALU/Shift micro-ops.
- ▶ Three more bits are required to control:


- ▶ Writing to the registers (RW)

- ▶ MUX B (MB)

- ▶ MUX D (MD)

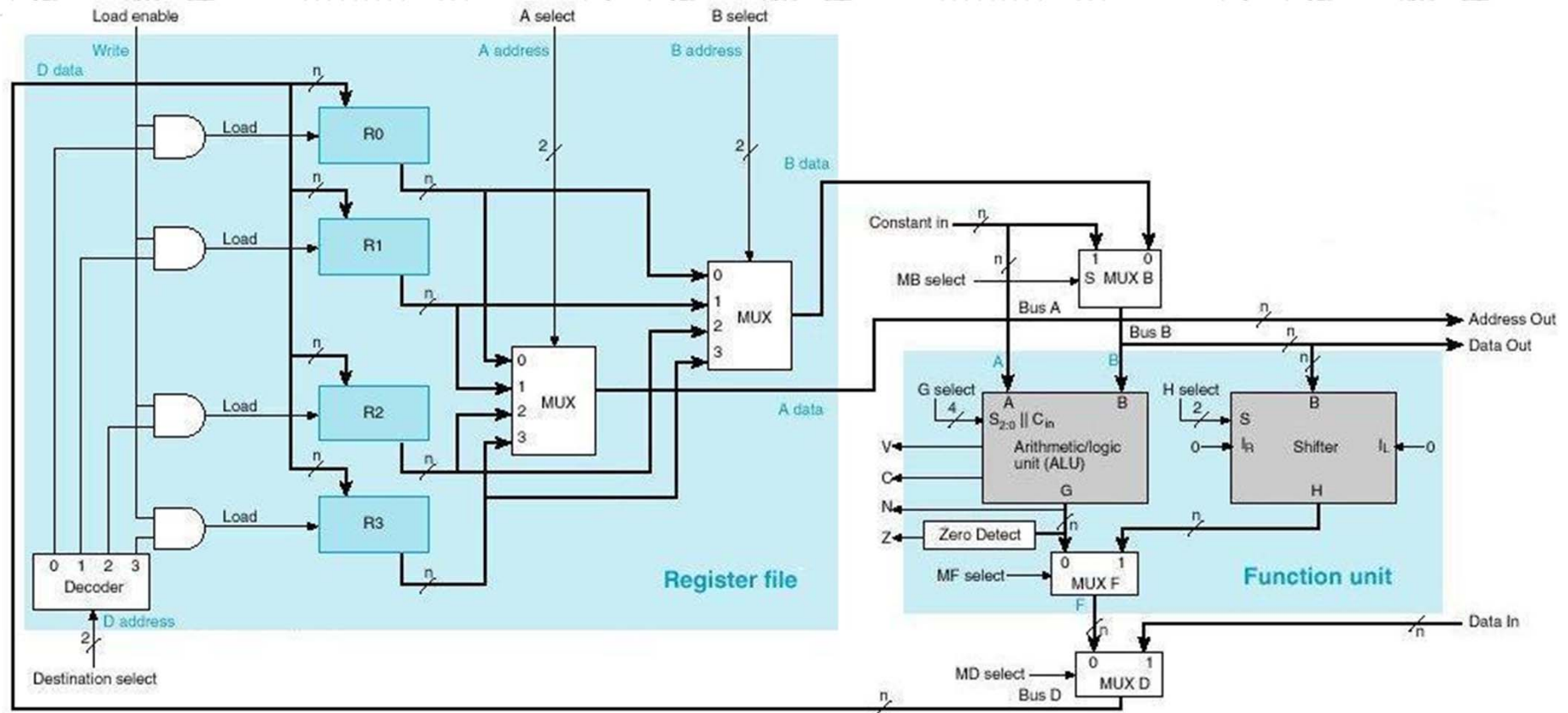


CS2022 Updated Datapath

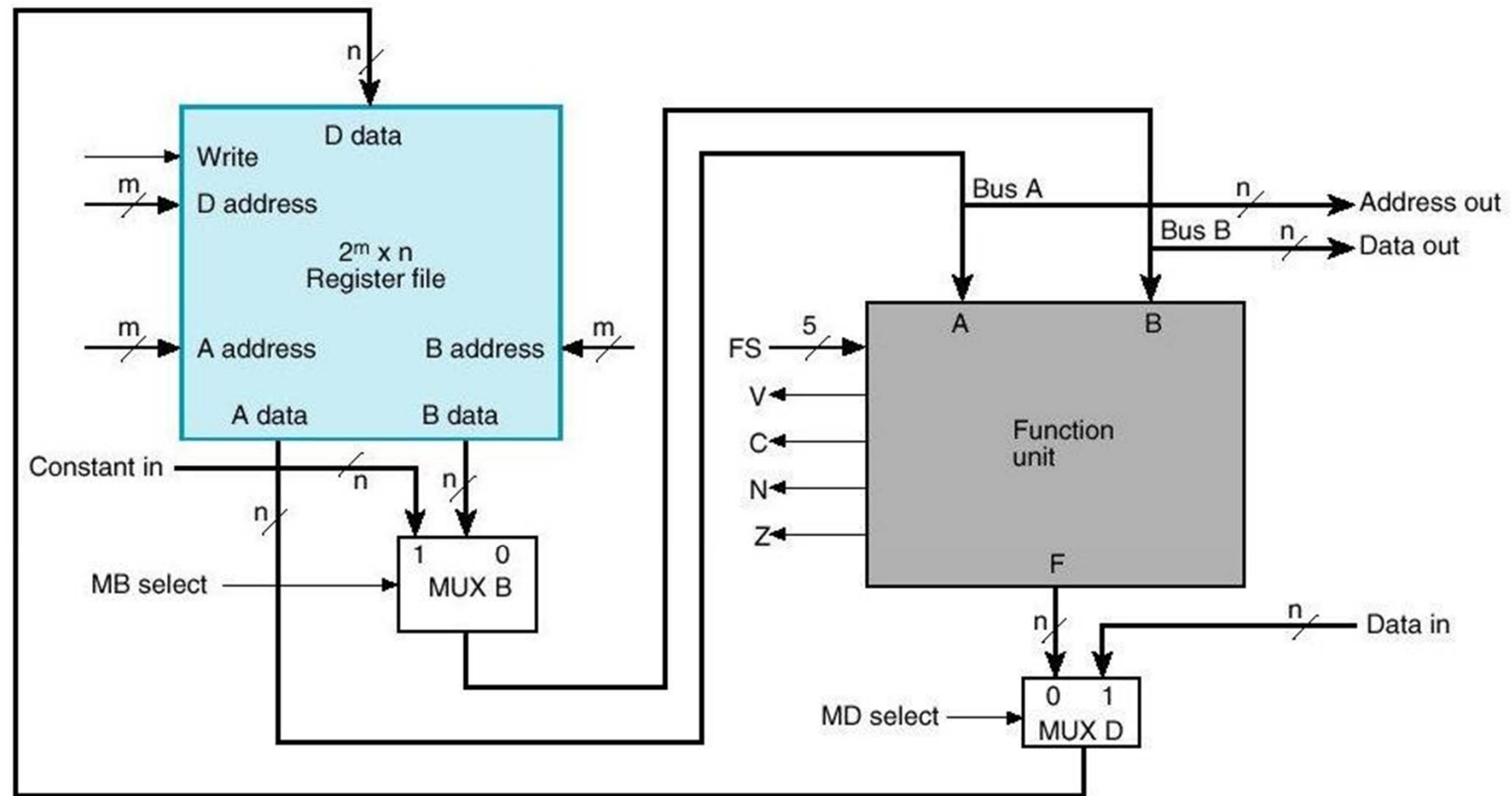

CS2022 Control Word

▶ The schematic on the next slide identifies all these control inputs and arranges them in a 17-bit vector called the Control Word.

CS2022 Datapath and the Control Word

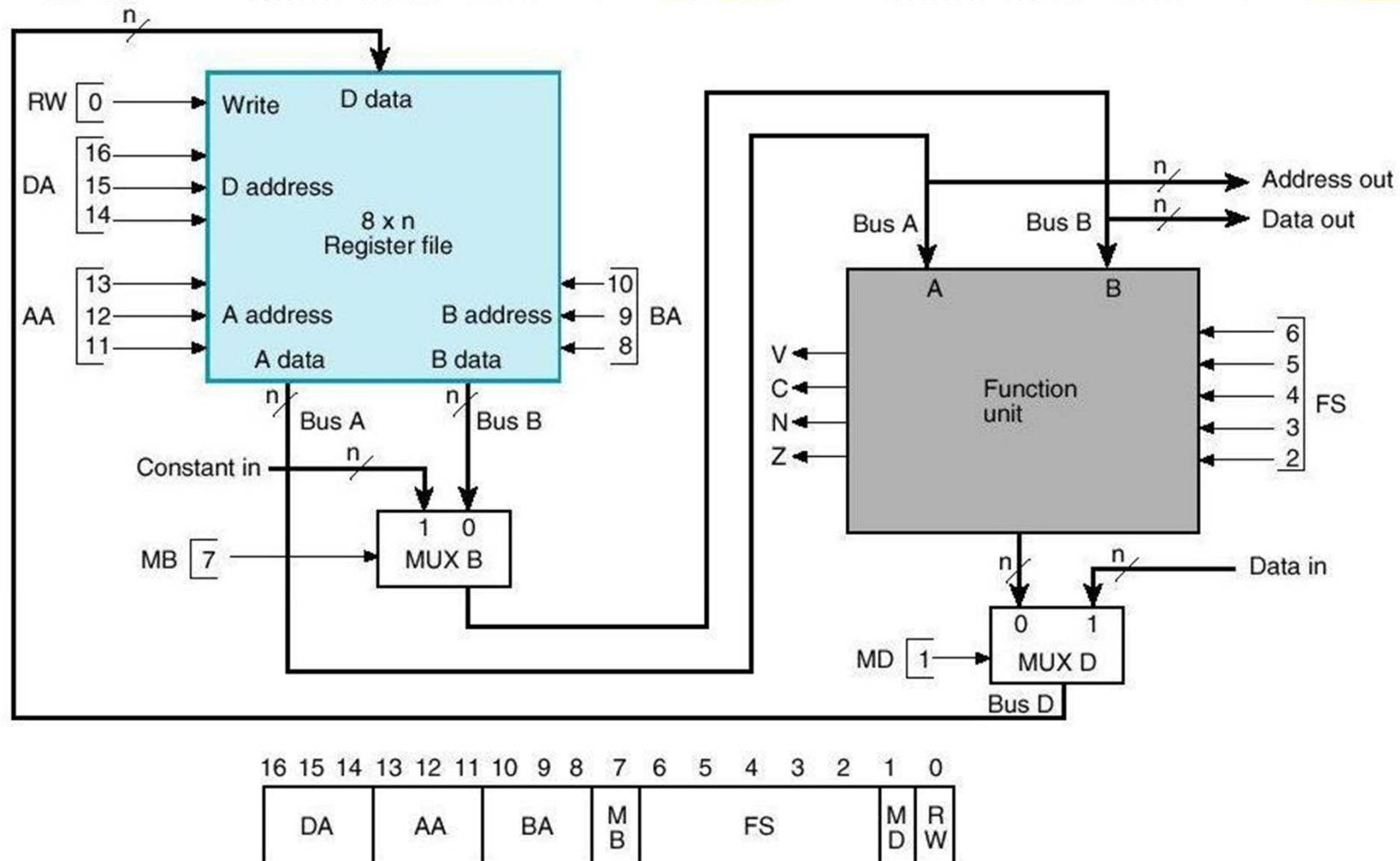

CS2022

The Control Word Specifies One Micro-ops




► Note that for the function select FS we need to make explicit the relationship between its value and the micro-ops.

► See next slide for details.

CS2022 **G** Select, **H** Select and **MF** Select determine the **FS** code


FS	MF Select	G Select	H Select	Output	
00000	0	0000	XX	$G = A$	TRANSFER
00001	0	0001	XX	$G = A + 1$	INCREMENT
00010	0	0010	XX	$G = A + B$	ADD
00011	0	0011	XX	$G = A + B + 1$	ADD WITH C
00100	0	0100	XX	$G = A + \underline{B}$	A plus 1's C.B
00101	0	0101	XX	$G = A + B + 1$	SUBTRACT
00110	0	0110	XX	$G = A - 1$	DECREMENT
00111	0	0111	XX	$G = A$	TRANSFER
01000	0	1000	XX	$G = A \wedge B$	AND
01010	0	1010	XX	$G = A \vee B$	OR
01100	0	1100	XX	$G = A \oplus B$	XOR
01110	0	1110	XX	$G = A$	NOT
10000	1	XXXX	00	$G = B$	TRANSFER
10100	1	XXXX	01	$G = sr B$	SHIFT RIGTH
11000	1	XXXX	10	$G = sl B$	SHIFT LEFT

CS2022 FS[2]=C_{in}

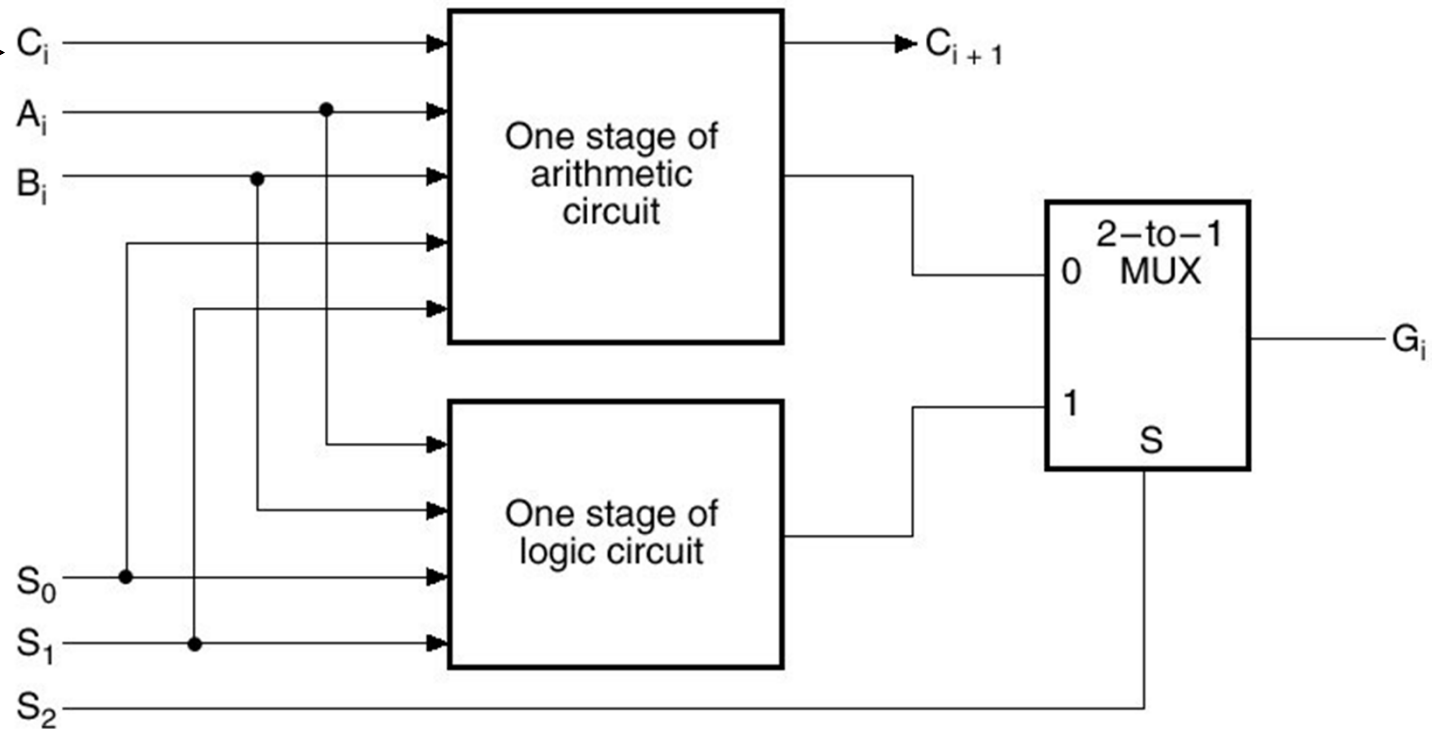


CS2022

$$FS[3 \wedge 4] = S_0 S_1$$

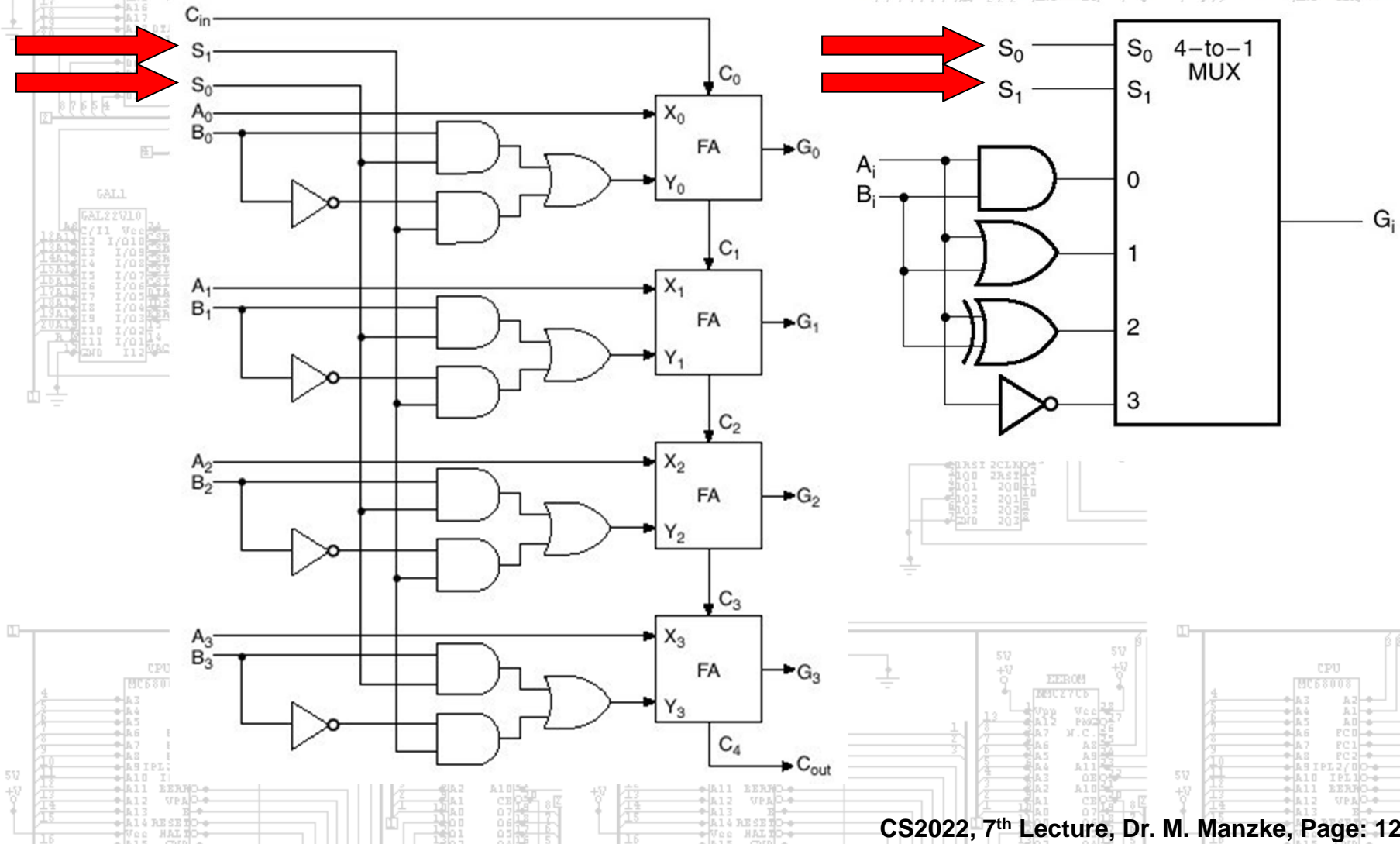

CS2022

$$FS[5] = S_2$$

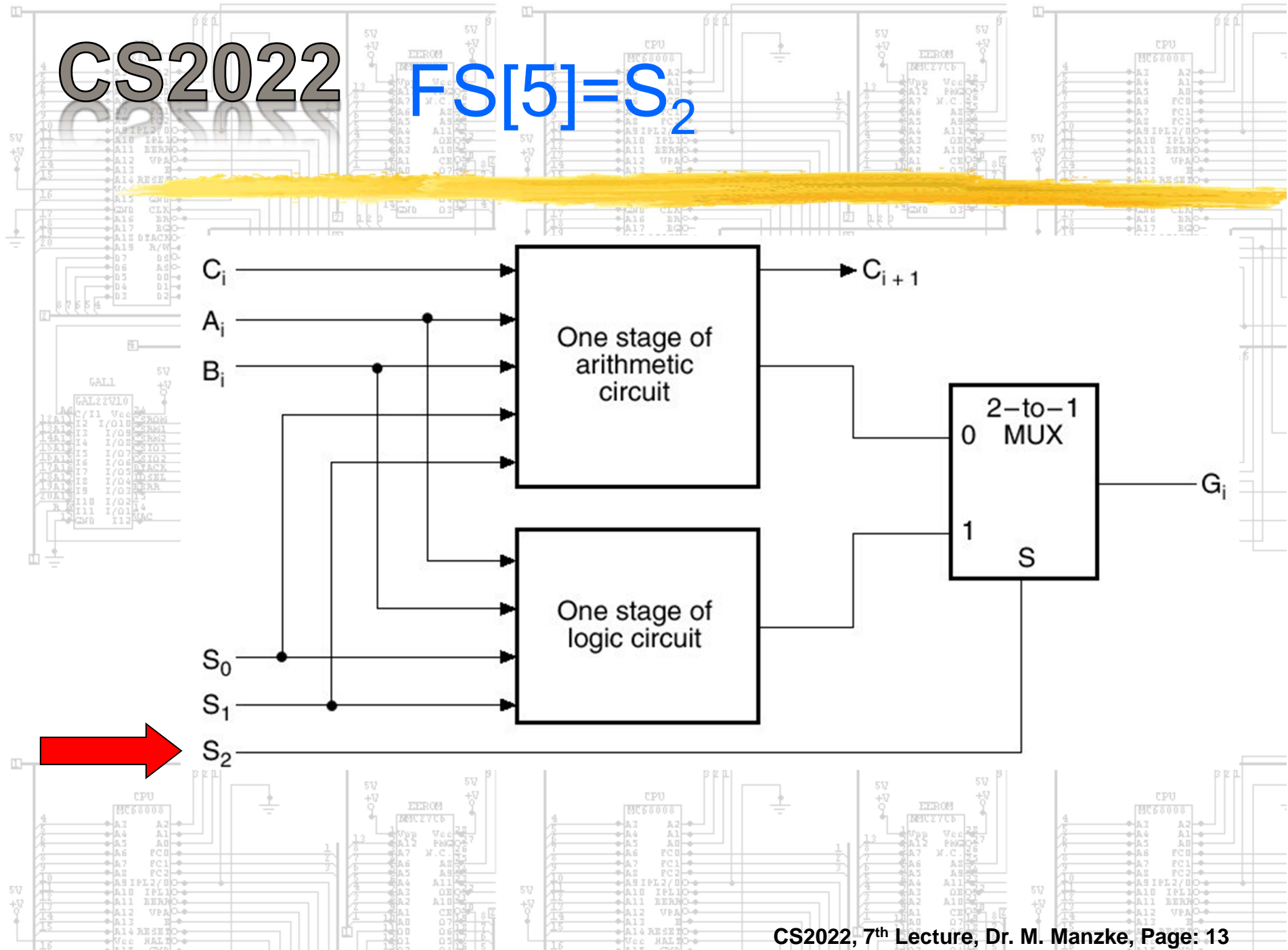

CS2022

$FS[6] = MF \text{ select}$

